
#### Spirit Level Reaction Time Tester


#### Group 52

Asmita Limaye Athreya Krishnan S. K. Anusri Prabodh Kant Rai Saurav Shukla Varun Singh


#### Inputs

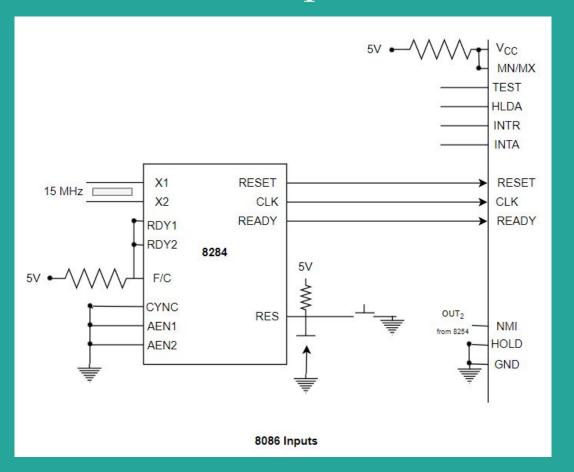


### System Bus of 8086 (Address)

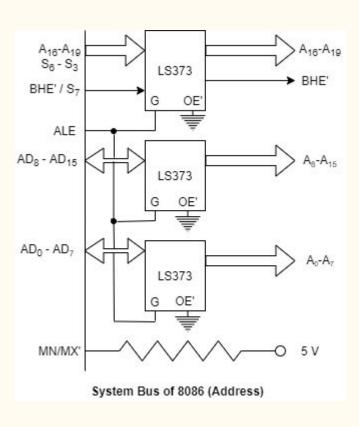

## System Bus of 8086 (Data + Control)

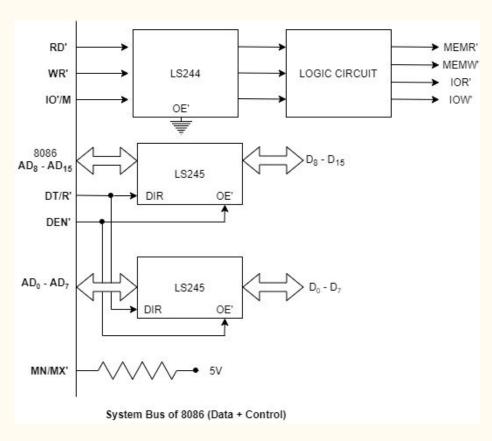


# Logic Circuit

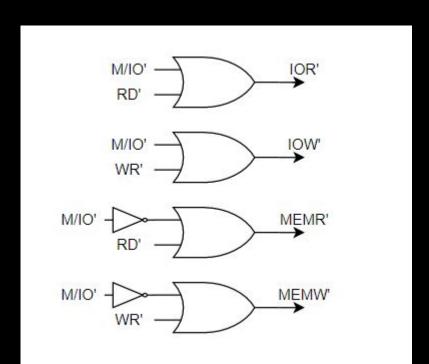


M/IO'	RD'	WR'	Bus Cycle
1	0	1	MEMR'
1	1	0	MEMW'
0	0	1	IOR'
0	1	0	IOW'

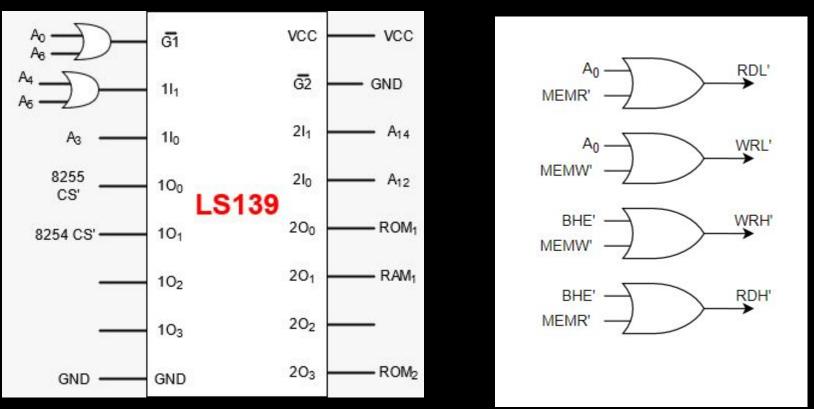
# Memory and I/O Decoder (Dual 2x4 decoder)




#### Memory Interfacing

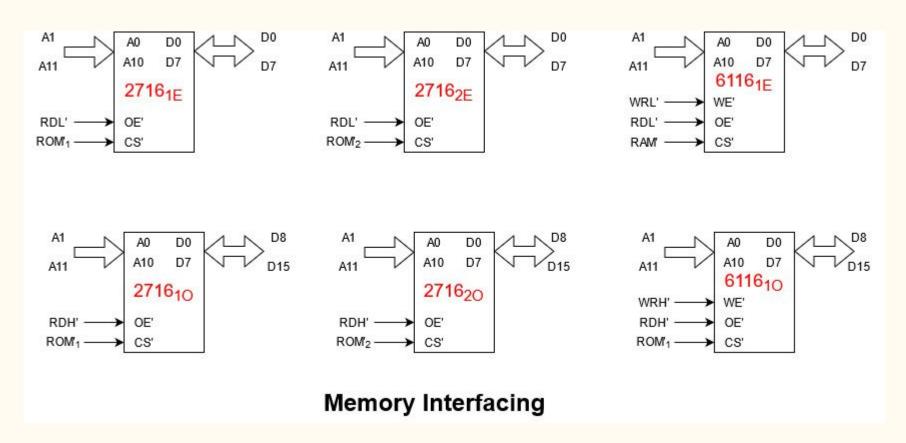


#### 8254 Interface to the Processor

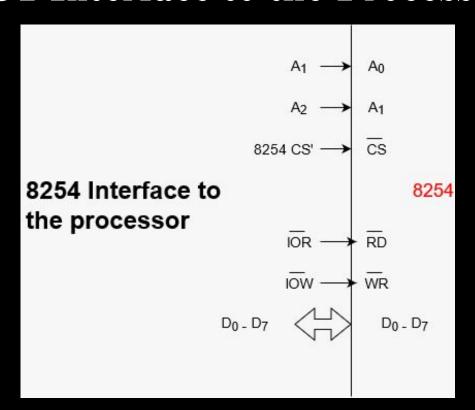


#### 

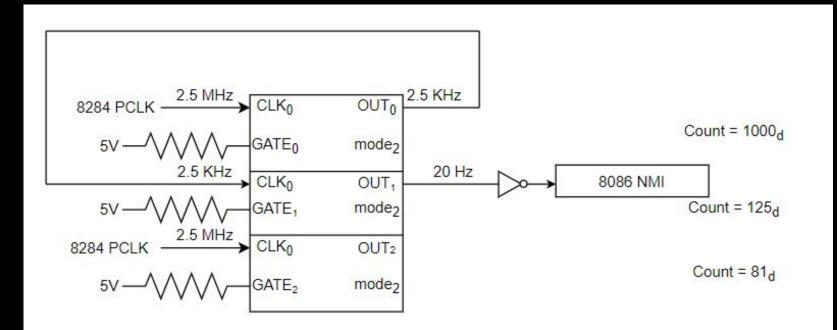

#### 8255 Interface to the Processor

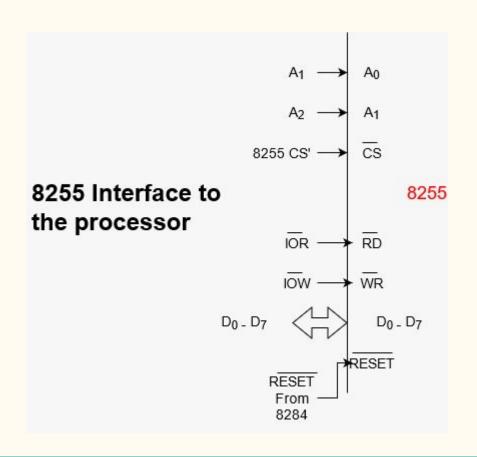

# 7 Segment Display Interfacing

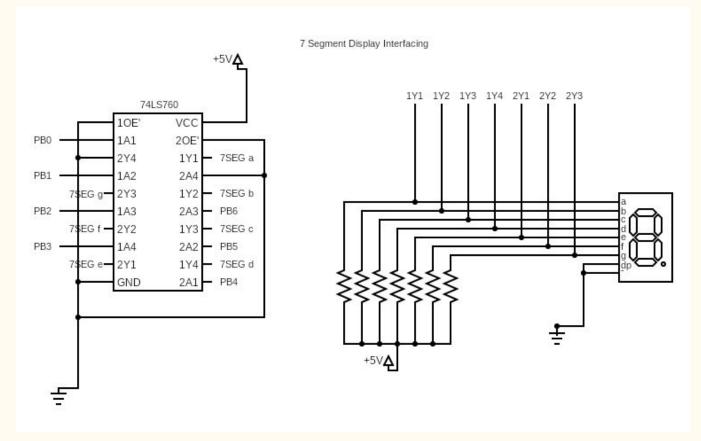

# 8255, LED, Button Interfacing

